

# ECE243


I/O Hardware

Prof. Enright Jerger

## Basic Components

### MULTIPLEXER

select	out
0	In 1
1	In 2


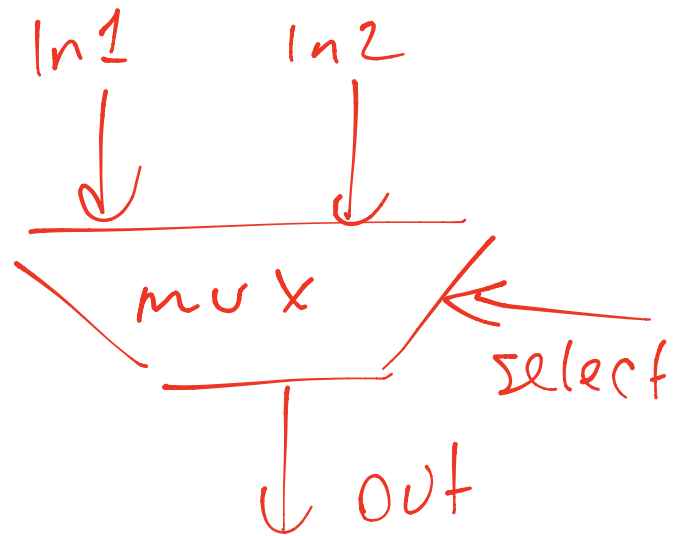


### DECODER

- Example: a 2->4 decoder

In(1)	In(0)	Out(3)	Out(2)	Out(1)	Out(0)
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


 
 
Can be used to match a specific value: eg., in==2?



## TRI STATE INTERFACE


- aka tri-state buffer
- used for attaching to shared wires
  - eg a bus
- Z = “high impedance”
  - ie no impact on outgoing wire

Enable	In	Out
1	0	0
1	1	1
0	0/1	Z

   

 
## PULL DOWN LINE

- normally made with a pull-up resistor
- resistor connected to power
  - pulls the line 'up' to 1 by default
- devices can pull the line 'down' to 0




# PASS TRANSISTOR

Enable	In	Out
1	0	0
1	1	1
0	0/1	z

 

 
## D/Q Flip Flop

- eg., rising edge triggered
- Like posing for a picture
  - Set-up time
    - say cheese and hold the pose
  - Hold-time
    - like taking a long exposure shot at night
- Q is set to D's value
  - when clk goes from low to high
- D must be stable for setup-time seconds
  - before the clock edge
- D must remain stable for hold-time seconds
  - after clock edge


 
# REGISTER

- stores an N-bit value
- is composed of N flip flops
- value is read/written in parallel




$\downarrow$   
 $out(N-1)$

$\downarrow$   
 $out(0)$
 
# SHIFT REGISTER


- stores an N-bit value
- composed of N flip flops
- value is read/written 1-bit at a time (serial)



## I/O Implementation
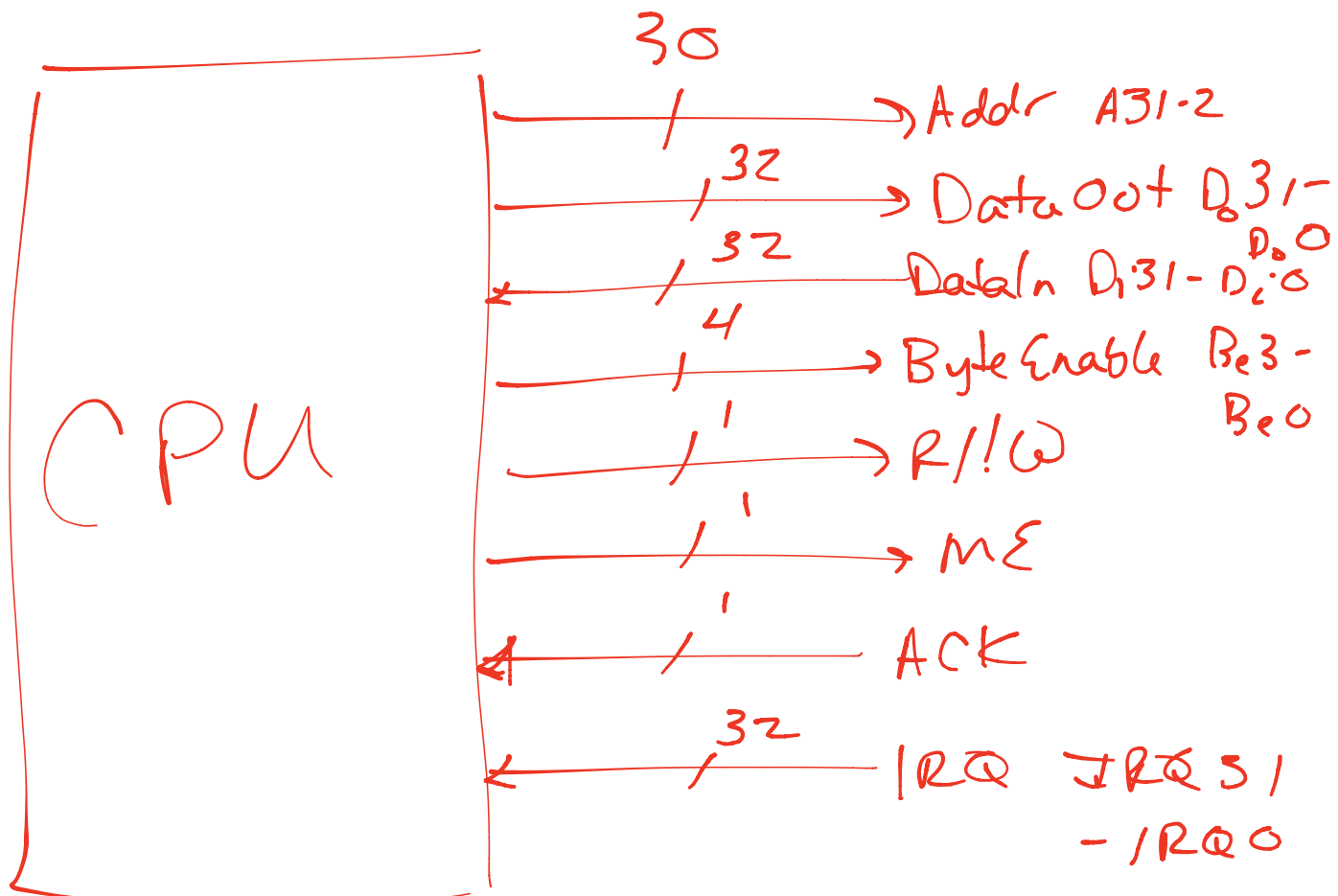
# NIOS Bus

- addr: only upper 30 bits: A31-A2 (missing A1-A0)
- byte enable: four wires, be3-be0
  - encodes two things: A1, A0 and word/halfword/byte
  - each wire indicates whether that byte is valid
- ME: master enable: one wire
  - do nothing if zero (avoid interpreting transient values)
- Ack: device sets this to one to ack processor request
- IRQ: set to one to request an interrupt



## BYTE-ENABLE Examples

	<u>a31-a2</u>	<u>a1-a0</u>	<u>be3-be0</u>	<u>di31-di0</u>
<u>Ldw</u>	0b100001	<u>00</u>	1111	di31-di0
<u>Ldb</u>	0b100001	<u>00</u>	0001	di7-di0
Ldb	0b101011	<u>01</u>	0010	di15-di8
Ldb	0b100101	10	0100	di23-di16
Ldb	0b101001	11	1000	di31-di24
<u>Ldh</u>	0b110101	<u>00</u>	0011	di15-di0
<u>Ldh</u>	0b110001	<u>10</u>	1100	di31-di16

## STEPS for a LOAD (protocol):

### 1) CPU:

- set addr, byte-enable, R/!W to 1;
- then set ME to 1

### 2) dev/mem:

- set DataIn to value
- set ACK to 1

### 3) CPU

- read DataIn lines
- set ME to 0

### 4) dev/mem:

- set ACK to 0



# STEPS for a store

## 1) CPU:

- set addr, byte-enable, DataOut, R/!W to 0;
- then set ME to 1

## 2) dev/mem:

- use DataOut values to update state
- set ACK to 1

## 3) CPU

- set ME to 0

## 4) dev/mem:

- set ACK to 0

# IMAGINARY I/O DEVICE

.equ MYDEVICE, 0xffabc0

0(MYDEVICE): <sup>32</sup>~~8~~bit input register

4(MYDEVICE): <sup>32</sup>~~8~~bit output register

Note: 0xffabc0 >> 2 = 0x3feaf0

value on  
A31-A2


(dropping A1, A0)

# READING A DEVICE REG:

```
.equ MYDEVICE, 0xffabc0
```

```
movia r8, MYDEVICE
```

```
ldwio r9,0(r8)
```

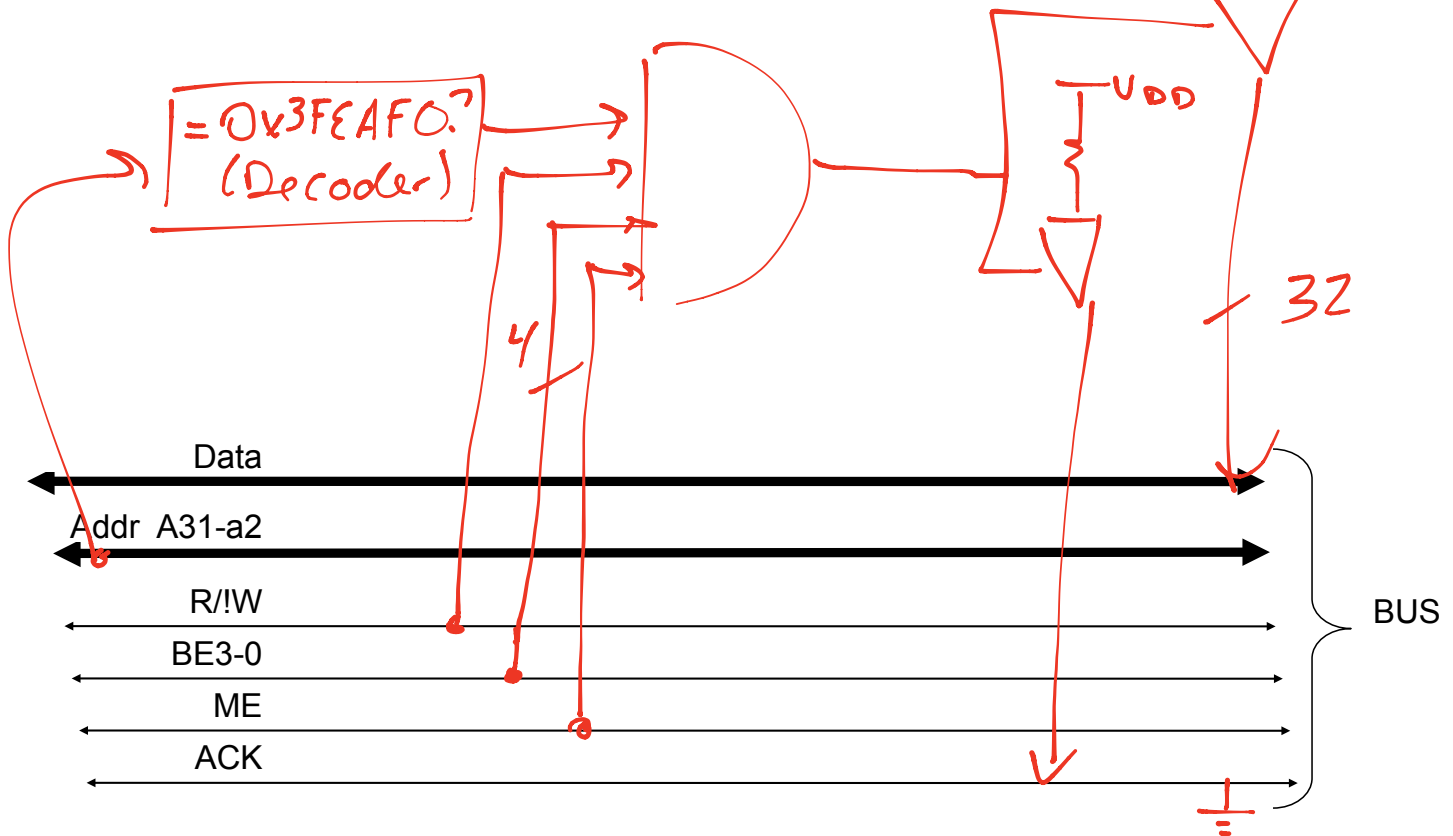


# WRITING A DEVICE REG:

```
equ MYDEVICE, 0xffabc0
```

```
movia r8, MYDEVICE
```

```
stwio r9,4(r8)
```

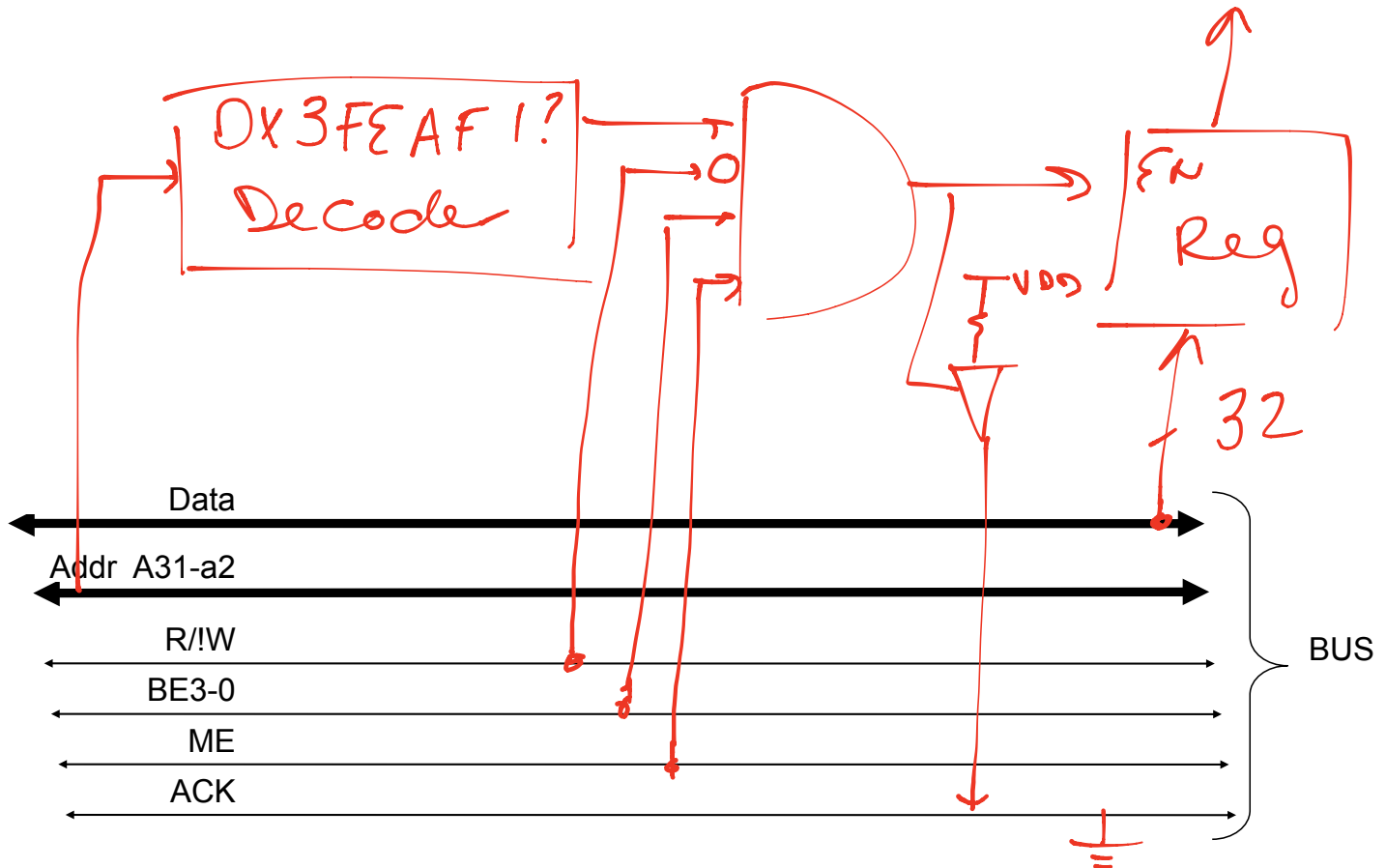

# PARALLEL INTERFACE

- **RECALL:**

.equ JP1, 0x10000060

0(JP1): data in/out DIO (<sup>32</sup>~~8~~ bits)

4(JP1): data direction register DIR, each bit configures data pin  
as in or out (<sup>32</sup>~~8~~ bits)

0 means input, 1 means out

0x10000060 >> 2 = 0x4000018


0x10000064 >> 2 = 0x4000019

# PARALLEL INTERFACE

JP1:

0(0x10000060): DIO # 0x10000060 >> 2 = 0x4000018

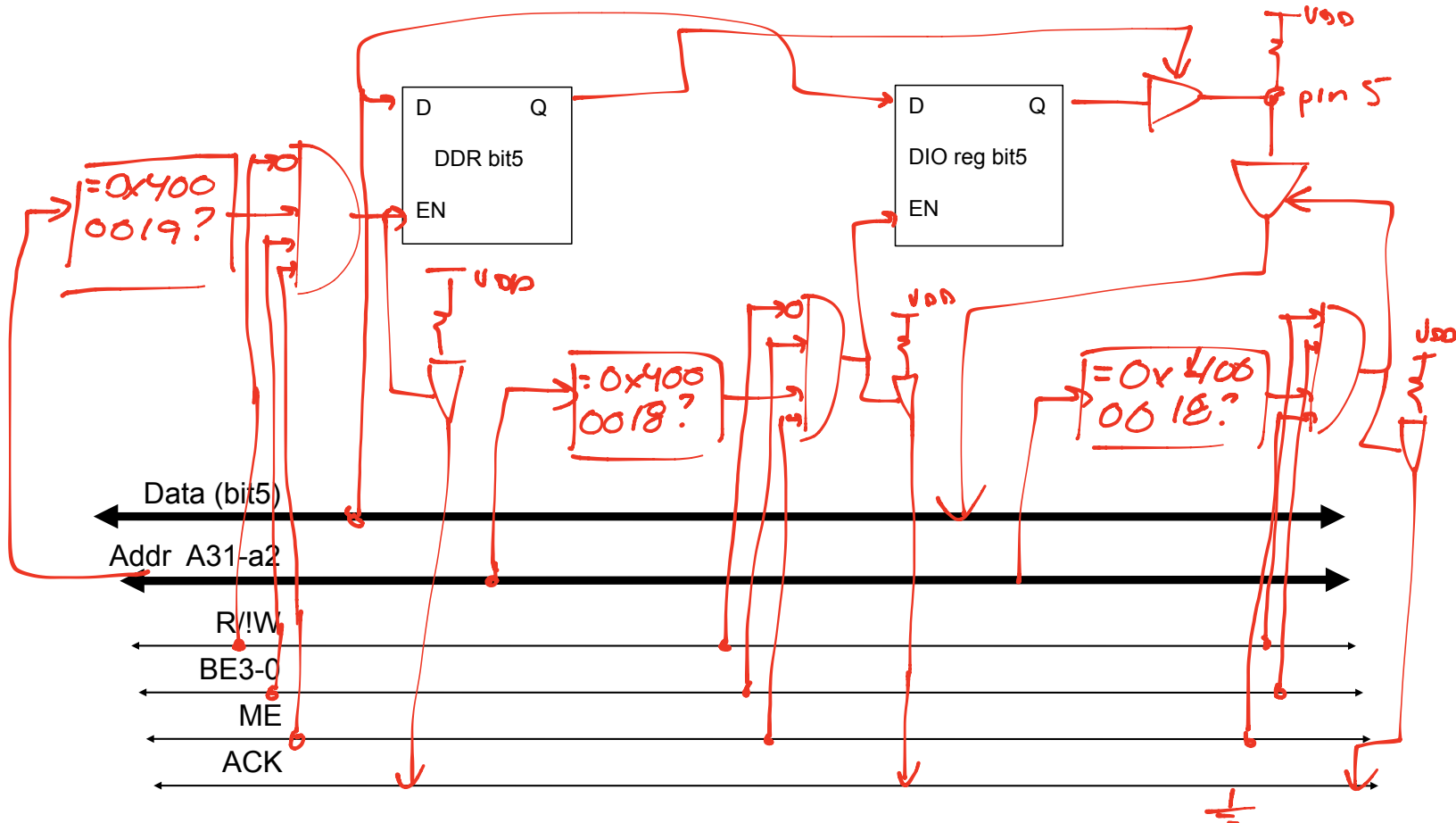
4(0x10000060): DIR # 0x10000060 >> 2 = 0x4000019




# Serial Interface

- Problem: single pin, but read/write bytes
- Solution: use shift registers


## Serial Input:

 

## Serial Output:

 

# Serial Interface: RS232

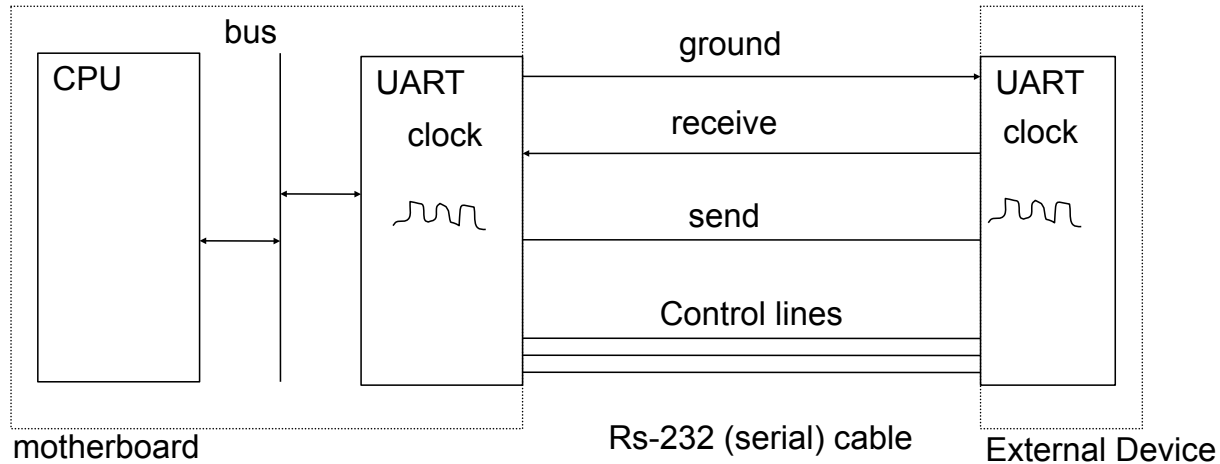

## SYNCHRONIZATION:

- each side has its own clock
- this causes problems:
  - clocks may not be exactly same speed



- ie., there is a frequency difference
- clocks may be out-of-sync
  - ie., there is a phase difference
- hardware has to handle these difficulties

# SERIAL TRANSMISSION

## 1. Both sides agree on a configuration:

- baud rate (bits per second)
- number of bits per group (7 or 8)
- is the MS-bit a parity bit? (odd or even)
- number of stop bits (1, 2...)
  - normally zero's

## 2. Can then send frames of bits

- start bit: normally a zero
- frame: 1 start bit + bit group + stop bits
- expect a new bit every period
  - $\text{period} = 1 / \text{baud-rate}$

# PARITY:

- Even parity:
  - the number of bits that are one is even
- Odd parity:
  - the number of bits that are one is odd
- Parity bit:
  - a bit that is added to ensure even or odd parity
  - typically the MSbit
- Ex: what is the parity bit for 1001110
  - even parity: 0
  - odd parity: 1
- Parity bit can be used to detect errors
  - Eg., if expecting even parity and get odd parity

## EXAMPLE CONFIGURATION:

- Baud rate: 1Kbaud = 1000 bits/s
  - #bits = 8
  - parity? = yes, even
  - # stop bits = 2 (stop bits are 1)
  - send ascii char: 011 0110
    - assume sends LSbit first
- frame: *start* 0 *data* 0 1 1 0 1 1 0 *parity* 0 *stop* 1 1
- earliest start new frame* ↙
- 
- start* *data* *parity* *stop*

## EFFECTIVE DATA RATE

- of 1k bits/s, some are wasted:
  - start bits, stop bits, parity bits
- Effective data rate:
  - the bit rate of non-wasted bits

- Ex: what is the effective data rate from previous example?

frac of useful bits = useful bits / total bits

$$7 / (1 + 7 + 1 + 2) = 7 / 11$$

$$7 / 11 \text{ Kbits/sec}$$